

# **FUNDAMENTALS OF VLSI DESIGN**

*(19EC6DCFOV)*

# Module-2

**Circuit Design Processes:** MOS layers, Stick diagrams, Design rules and layout – lambda-based design and other rules. Examples. (Text book-1)

**CMOS Sub System Design:** Introduction, Addition/Subtraction, Single bit addition, Full adder design, Comparators, LFSR,XOR/XNOR circuits (Text book-3)

## **Text books:**

1. Douglas A. Pucknell, Kamran E., “Basic VLSI Design”, 3<sup>rd</sup> Edition, *PHI Publication*, India.
3. Neil H.E. Weste, Harris, Banerjee, “CMOS VLSI design”, *Pearson*, Third Edition, 2007.













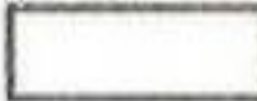
# MOS LAYERS

- MOS design aim – **turning a specification into masks** for processing silicon to meet the specification.
- Four basic layers
  - n- diffusion
  - p- diffusion
  - Polysilicon
  - Metal
- **Isolated from one another** by thick or thin (thinox) silicon dioxide insulating layers.
- **Polysilicon and thinox regions interact** so that a **transistor is formed** where they cross one another.
- The **thin oxide (thinox) mask region** includes **n-diffusion, p-diffusion, and transistor channels.**
- **Contacts** are **used to join the layers**












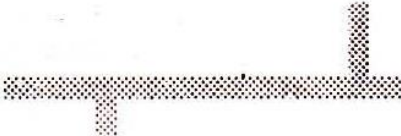

# STICK DIAGRAMS

- Stick diagrams are used **to convey layer information through the use of a colour code.**
- Example, for CMOS design,
  - green for n-diffusion
  - Yellow/Brown for p-diffusion
  - red for polysilicon
  - blue for metal
  - black for contact areas
- **Color coding** has been **complemented by monochrome encoding** of the lines.


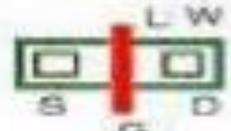
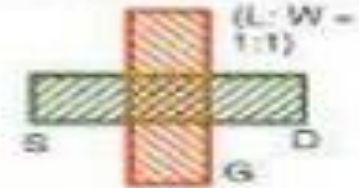



# NMOS technology

COLOR	STICK ENCODING	LAYERS	MASK LAYOUT ENCODING
GREEN		n-diffusion (n <sup>+</sup> active) Thin <sub>ox</sub> *	 *Thin <sub>ox</sub> = n-diff. + transistor channels
RED		Polysilicon	
BLUE		Metal 1	
BLACK		Contact cut	
GRAY	NOT APPLICABLE	Overglass	
nMOS ONLY YELLOW		Implant	
nMOS ONLY BROWN		Buried contact	

# Encodings for a simple metal nMOS process







COLOR	STICK ENCODING	LAYERS	MASK LAYOUT ENCODING
	MONOCHROME		MONOCHROME
GREEN		n-diffusion (n <sup>+</sup> active) Thinox *	 * Thinox = n-diff. + transistor channels
RED		Polysilicon	
BLUE		Metal 1	
BLACK		Contact cut	
GRAY	NOT APPLICABLE	Overglass	
nMOS ONLY YELLOW		Implant	
nMOS ONLY BROWN		Buried contact	

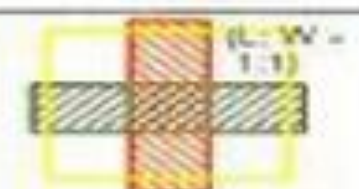

FEATURE	FEATURE (STICK)	FEATURE (SYMBOL)	FEATURE (MASK)
n-type enhancement mode transistor			
n-type depletion mode transistor nMOS only			

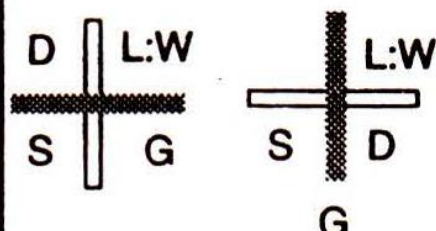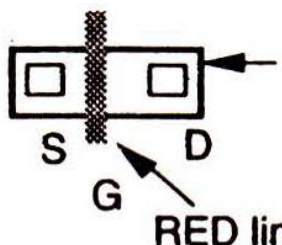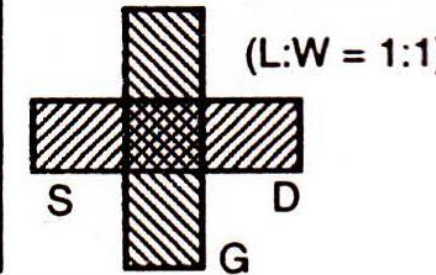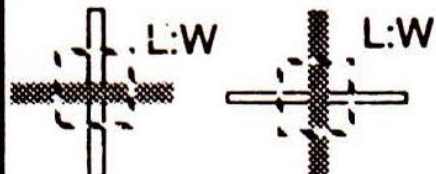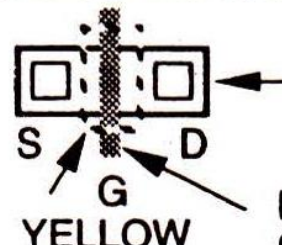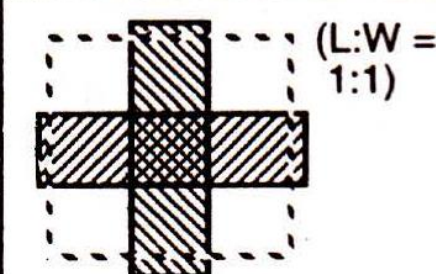
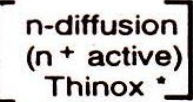





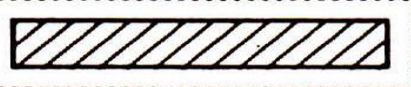

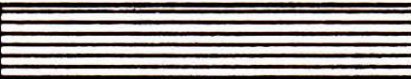



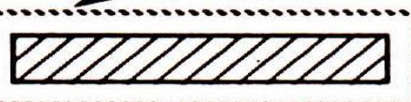
Transistor length to width ratio L:W should be shown.

Source, drain and gate labeling will not normally be shown.

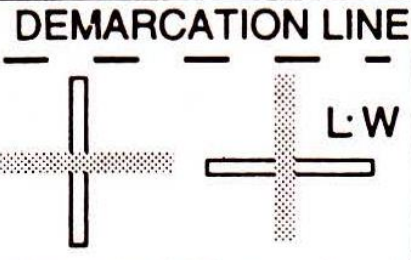
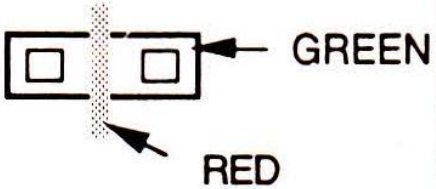
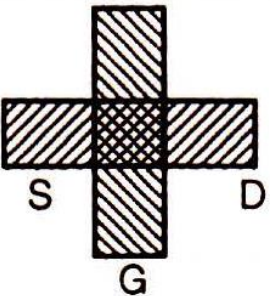

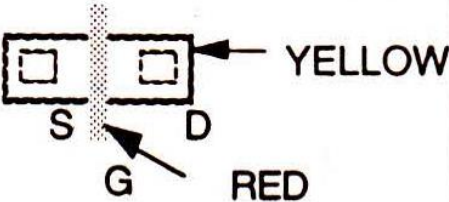
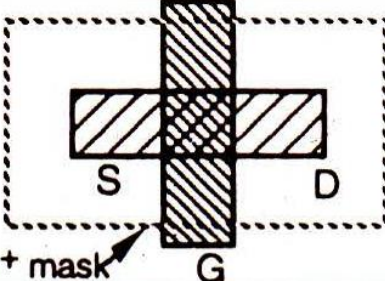
FEATURE	FEATURE (STICK) (MONOCHROME)	FEATURE (SYMBOL) (MONOCHROME)	FEATURE (MASK) (MONOCHROME)
<i>n-type enhancement mode transistor</i>		 GREEN outline (COLOR) RED line (COLOR)	
<i>n-type depletion mode transistor</i> <b>nMOS ONLY</b>		 GREEN outline (COLOR) RED line (COLOR) YELLOW (COLOR)	

Transistor length to width ratio L:W should be shown but source, drain and gate labeling will not normally be shown.

# Encodings for CMOS process

COLOR	STICK ENCODING	LAYERS	MASK LAYOUT ENCODING
GREEN	<b>MONOCHROME</b>    <b>ENCODING AS IN FIGURE 3-1(a)</b>	 • Thinox = n-diff. + p-diff. + transistor channels	<b>MONOCHROME</b>    <b>ENCODING AS IN FIGURE 3-1(a)</b>
RED		Polysilicon	
BLUE		Metal 1	
BLACK		Contact cut	
GRAY		Overglass	
GREEN IN P <sup>+</sup> (MASK)	  <b>NOT SHOWN IN STICK DIAGRAM</b>      <b>DEMARCATON LINE</b> p-well edge is shown as a demarcation line in stick diagrams  	p-diffusion (p <sup>+</sup> active)	      
YELLOW (STICK)		p <sup>+</sup> mask	
YELLOW			
DARK BLUE OR PURPLE		Metal 2	
BLACK		VIA	
BROWN		p-well	
BLACK		V <sub>DD</sub> or V <sub>SS</sub> CONTACT	V <sub>DD</sub> V <sub>SS</sub>



FEATURE	FEATURE (STICK) (MONOCHROME)	FEATURE (SYMBOL) (MONOCHROME)	FEATURE (MASK) (MONOCHROME)
<i>n-type enhancement mode transistor</i>  (as in Figure 3-1(a) )  Transistor length to width ratio L:W may be shown.			
<i>p-type enhancement mode transistor</i>  Note: p-type transistors are placed above and n-type transistors below the demarcation line			

# Steps for CMOS Process







- Draw the metal (Blue) Vdd and Vss rails in parallel and create a demarcation line between them. Allowing enough space between them for other circuit elements.
- N-Devices are placed below the demarcation line and P-device are placed above the demarcation line.
- N & P devices are then connected using metal, Polysilicon and contacts.
- Finally the remaining interconnections are made & control signals and data inputs are added.

# Introduction

- Stick diagrams convey layer information in a chip.
- Interface between the circuit and the layout.
- Size of transistors, width of layers, wire length etc... are not mentioned in a stick diagram.
- For a chip designer, all CMOS designs consist of the following layers:
  - Substrate or wells of p-type for nMOS transistors and n-type for pMOS transistors
  - Diffusion layers, generally called as Active areas
  - Polysilicon layers, forms the Gate terminals
  - Metal and interconnect layers
  - Contact and via layers




# Colour Codes & Patterns

Layers	Colour	Patterns
N diffusion	Green	
P diffusion	Yellow/Brown	
Polysilicon	Red	
Metal 1	Blue	
Metal 2	Magenta	
Contact & Taps	Black	


$V_{DD}$  and  $V_{SS}$  - metal layers - Blue

# Transistors using Colour Code

## NMOS Transistor


 


## PMOS Transistor

 



## Example - CMOS Inverter

  

# Important Note

- Diffusion paths must not cross the demarcation line.
- N & P diffusion wires must not join.
- The metal should be used to connect n & p features.
- We must place crosses (X) on Vdd and Vss rails to represent substrate and P-well connections respectively.
- Only metal & polysilicon can cross the demarcation line.
- Represent the Vss and Vdd contact crosses
  - One on Vdd line for every 4 P-transistors.
  - One on Vss line for every 4 N-transistors.
- Metal lines on different layers (M1 and M2) can cross one another. Contacting 2 metal lines requires a Via.

# Steps for NMOS Process

- Draw the metal Vdd and Vss rails in parallel and create a demarcation line between them. Allowing enough space between them for other circuit elements.
- Draw the diffusion paths between the rails.
- Pull up device (depletion type) is to be connected from the output point (Source) to Vdd (Drain)
- Pull down device (enhancement type) is to be connected from the output point (Drain) to Ground (Source)

# DESIGN RULES AND LAYOUT

- The **object** of a set of design rules is **to allow** a ready **translation of circuit design concepts**, usually **in stick diagram** or symbolic form, **into actual geometry in silicon**.
- The design rules are the **effective interface between the circuit/system designer and the fabrication engineer**.
- 2-ways
  - $\mu$  metal based design rules (orbit)
  - Lambda-based Design Rules
    - **straightforward**
    - **relatively simple to apply**

- Design rules are the communication link between the designer specific requirements and the fabricator (metalizing the design)
- Design rules are workable mask layers from which the various layer in silicon.



## Layout Design Rules


- ◆ **Width** - the minimum width of a rectangle
- ◆ **Spacing** - the minimum spacing between two rectangles on the same or different layers
- ◆ **Overlap** - specifies how much a rectangle must surround another on another layer

$$\lambda = \frac{\text{channel length (L)}}{2}$$

# Design Rules




METAL

 

DIFFUSION




POLYSILICON

 

# Design Rules




METAL

 

DIFFUSION




POLYSILICON

 

# Design Rules




METAL

 

DIFFUSION



POLYSILICON

 

# Design Rules



METAL





POLYSILICON

$\lambda$







# Design Rules

  


# Different layers for Layout

 


Poly Silicon

 


n-diff

 

p-diff

 


M1

 

M2


# Lambda-based Design Rules

 

**Figure 3–6** Design rules for wires (nMOS and CMOS)




## Minimum size transistors



 


# 1. Metal 1 to polysilicon or to diffusion

$3\lambda$  minimum

 

   
$2\lambda \times 2\lambda$  cut centered  
on  $4\lambda \times 4\lambda$  superimposed  
areas of layers to be joined  
in all cases



Minimum separation  
Multiple cuts

## 2. Via (contact from metal 2 to metal 1 and thence to other layers)

Metal 2

 


$2\lambda$  minimum separation  
(if other spacings allow)

$4\lambda \times 4\lambda$  area of overlap with  
 $2\lambda \times 2\lambda$  via at center

Metal 1

Via and cut used to  
connect metal 2 to  
diffusion

 

**FIGURE 3.8 Contacts (nMOS and CMOS).**



# CMOS Sub System Design

# Introduction

Partitioning the system into subsystems of the types listed below:


- Datapath operators
- Memory elements
- Control structures
- Special-purpose cells
  - I/O
  - Power distribution
  - Clock generation and distribution
  - Analog and RF

# Addition/Subtraction

- Basis for many processing operations- counting, multiplication, filtering etc..
- add two binary numbers
- adder architectures serve different speed/power/area requirements


## Single bit addition

### 1) Half adder

 


<i>A</i>	<i>B</i>	<i>C<sub>out</sub></i>	<i>S</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0
 
$$S = A \oplus B$$
$$C_{\text{out}} = A \cdot B$$



## 2) Full adder

 

A	B	C	G	P	K	C <sub>out</sub>	S
0	0	0	0	0	1	0	0
		1				0	1
0	1	0	0	1	0	0	1
		1				1	0
1	0	0	0	1	0	0	1
		1				1	0
1	1	0	1	0	0	1	0
		1				1	1

**Generate (G):** The adder generates a carry when Cout is true independent of Cin

$$G = A \cdot B.$$

**Propagate (P):** The adder propagates a carry; i.e., it produces a carry-out if and only if it receives a carry-in

$$P = A \oplus B.$$

**Kill (K):** The adder kills a carry when Cout is false independent of Cin

$$K = \bar{A} \cdot \bar{B} = \overline{A + B}$$

$A$	$B$	$C_i$	$S$	$C_o$	<i>Carry status</i>
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

For S:

# Full adder design

		$BC_{in}$			
$A$	$\overline{B}\overline{C}_{in}$	$\overline{B}C_{in}$	$BC_{in}$	$B\overline{C}_{in}$	
	$\overline{A}$	1		1	
$A$	1		1		

$$S = A \oplus B \oplus C_{in}$$

$$S = \overline{A}\overline{B}\overline{C}_{in} + \overline{A}B\overline{C}_{in} + A\overline{B}C_{in} + AB\overline{C}_{in}$$

$$S = \overline{A}\overline{B}\overline{C}_{in} \cdot \overline{A}\overline{B}C_{in} \cdot A\overline{B}C_{in} \cdot A\overline{B}\overline{C}_{in}$$
$$= (\overline{A} + \overline{B} + \overline{C}_{in}) \cdot (A + B + \overline{C}_{in}) \cdot (\overline{A} + \overline{B} + C_{in}) \cdot (A + B + C_{in})$$

		$BC_{in}$			
$A$	$\overline{A}$	$\overline{B}\overline{C}_{in}$	$\overline{B}C_{in}$	$BC_{in}$	$B\overline{C}_{in}$
	$A$		1	1	1

$$C_{out} = \overline{A}B + BC_{in} + C_{in}A$$

$$\begin{aligned}
 C_{out} &= \overline{A}B + \overline{B}C_{in} + \overline{C_{in}}A \\
 &= (\overline{A} + \overline{B}) \cdot (\overline{B} + \overline{C_{in}}) \cdot (\overline{C_{in}} + \overline{A})
 \end{aligned}$$



# Common procedure used for all type of circuits:

## NMOS


OR operation (+)  
AND operation (.)

**parallel**  
**series**

## PMOS

OR operation (+)  
AND operation (.)

**series**  
**parallel**


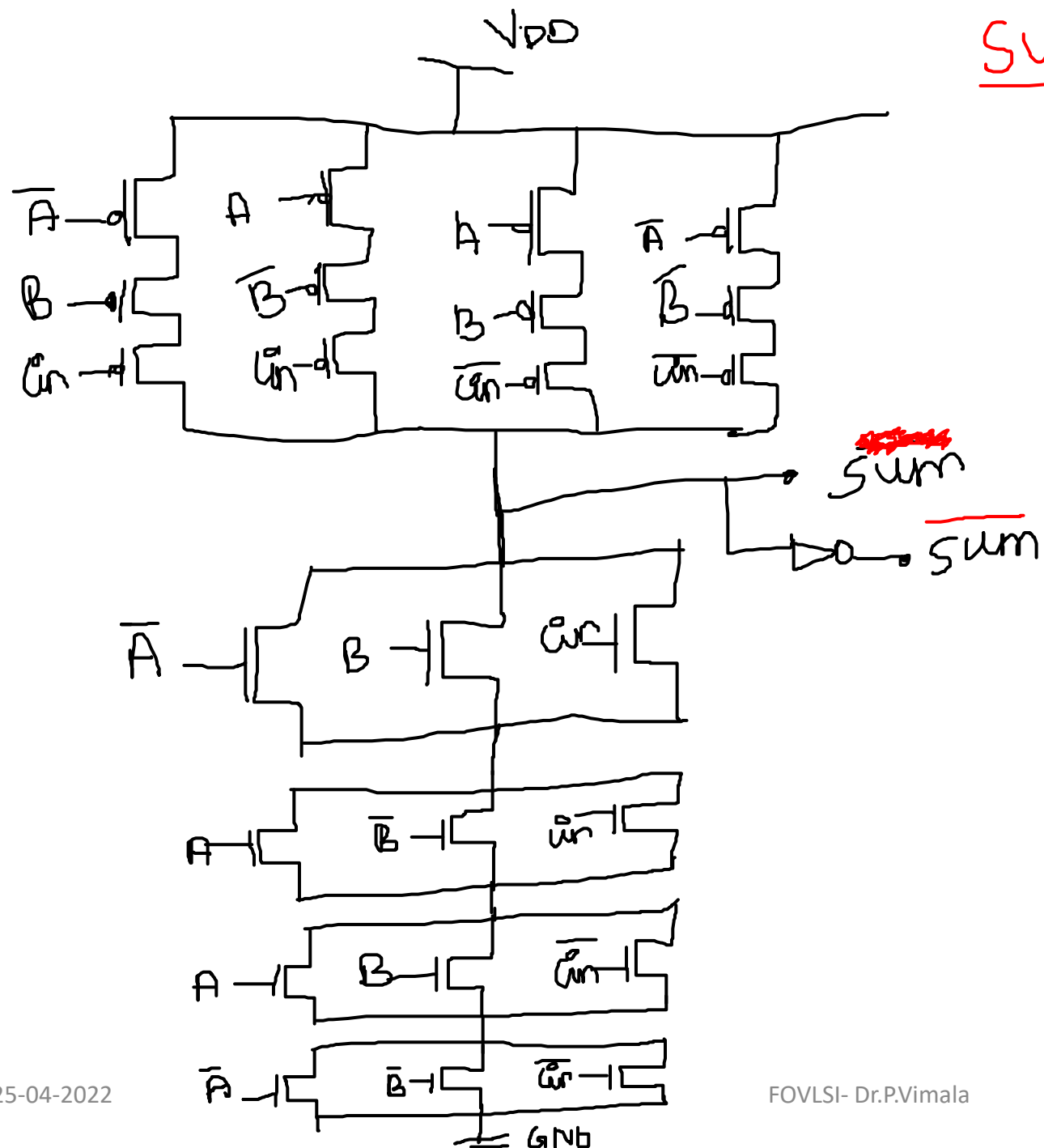


sum


No of transistors

24 ~~24~~


24

  

(a)

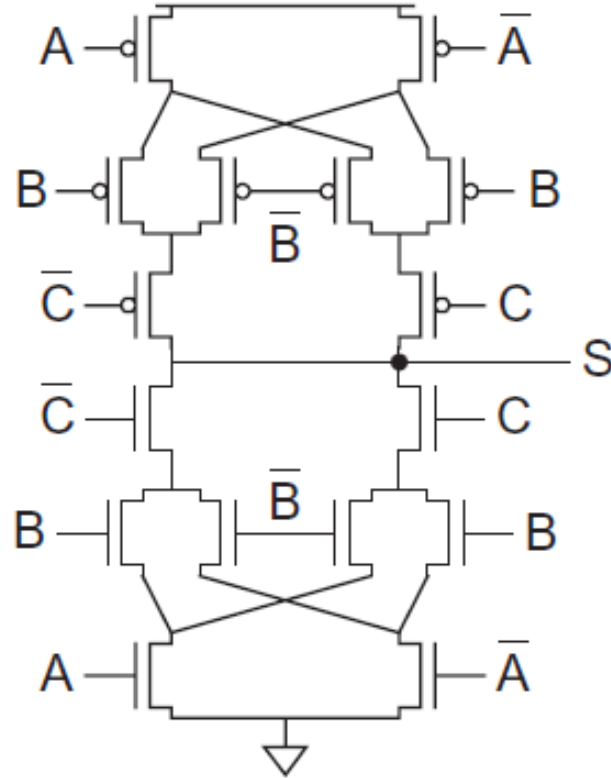

(b)

 

32 transistors (6 for the inverters, 10 for the majority gate, and 16 for the 3-input XOR).

A	B	C	G	P	K	C <sub>out</sub>	S
0	0	0	0	0	1	0	0
		1				0	1
0	1	0	0	1	0	0	1
		1				1	0
1	0	0	0	1	0	0	1
		1				1	0
1	1	0	1	0	0	1	0
		1				1	1

	BC <sub>in</sub>			
A	$\overline{B}\overline{C}_{in}$	$\overline{B}C_{in}$	$BC_{in}$	$B\overline{C}_{in}$
$\overline{A}$			1	
A		1	1	1

$$C_{out} = AB + BC_{in} + C_{in}A$$

$$C_{out} = AB + C_{in}(A + B) \checkmark$$

$$S = C_{in}\overline{C_{out}} + B\overline{C_{out}} + A\overline{C_{out}} + ABC_{in}$$


$$S = \overline{C_{out}}[A + B + C_{in}] + ABC_{in}$$


A	B	C <sub>in</sub>	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1 ✓
0	1	0	0	1 ✓
0	1	1	1	0
1	0	0	0	1 ✓
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1 ✓

$$C_{out} = AB + C_{in}(A+B)$$


$$S = AB\bar{C}_{in} + \bar{C}_{out}(A+B+C_{in})$$

28

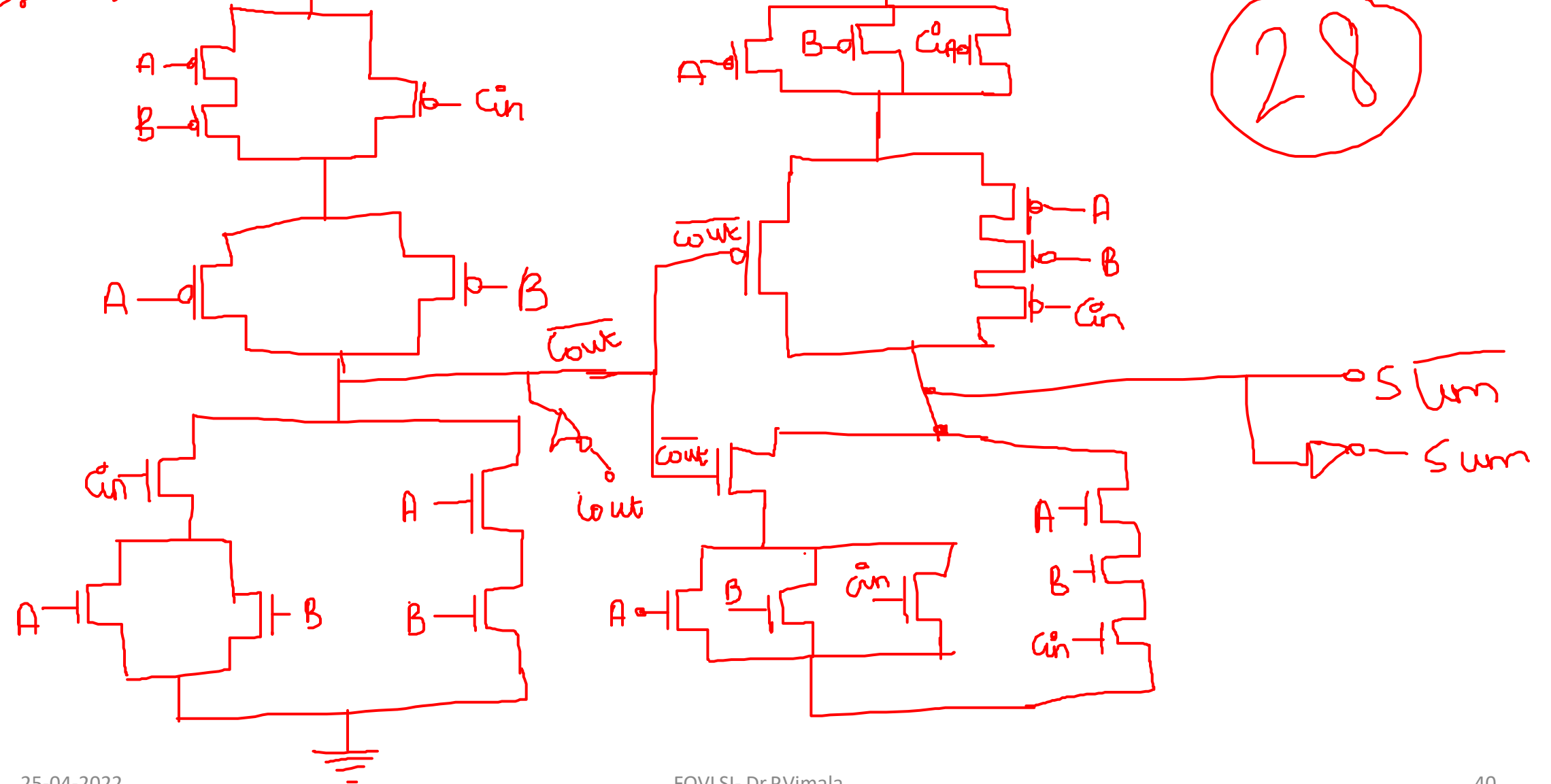

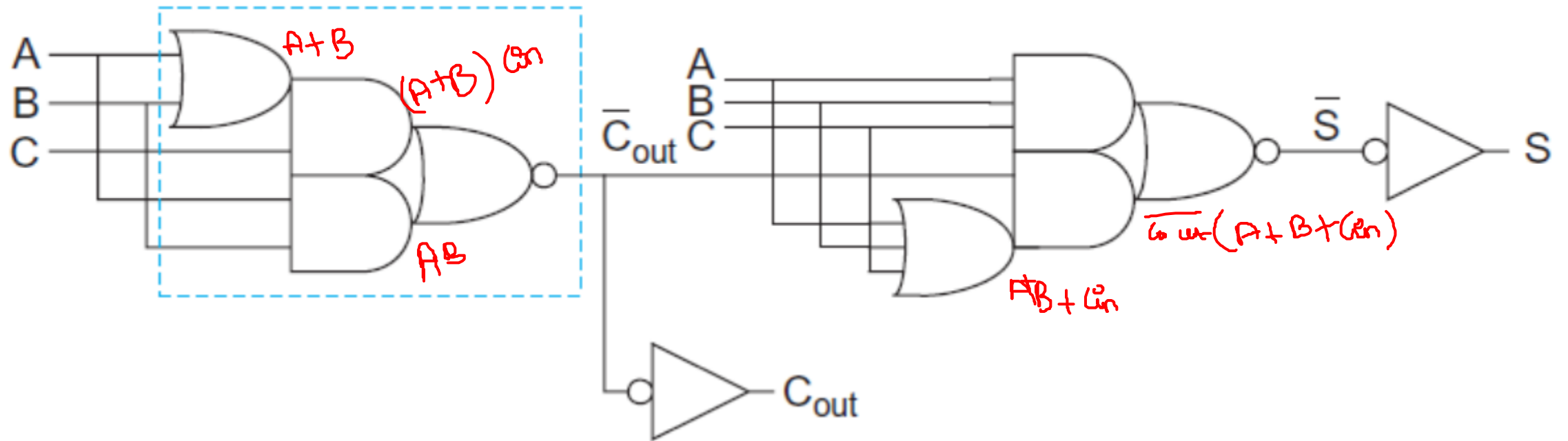



 


pMOS network is identical to the nMOS network rather than being the conduction complement, so the topology is called a **mirror adder**.

# Comparators
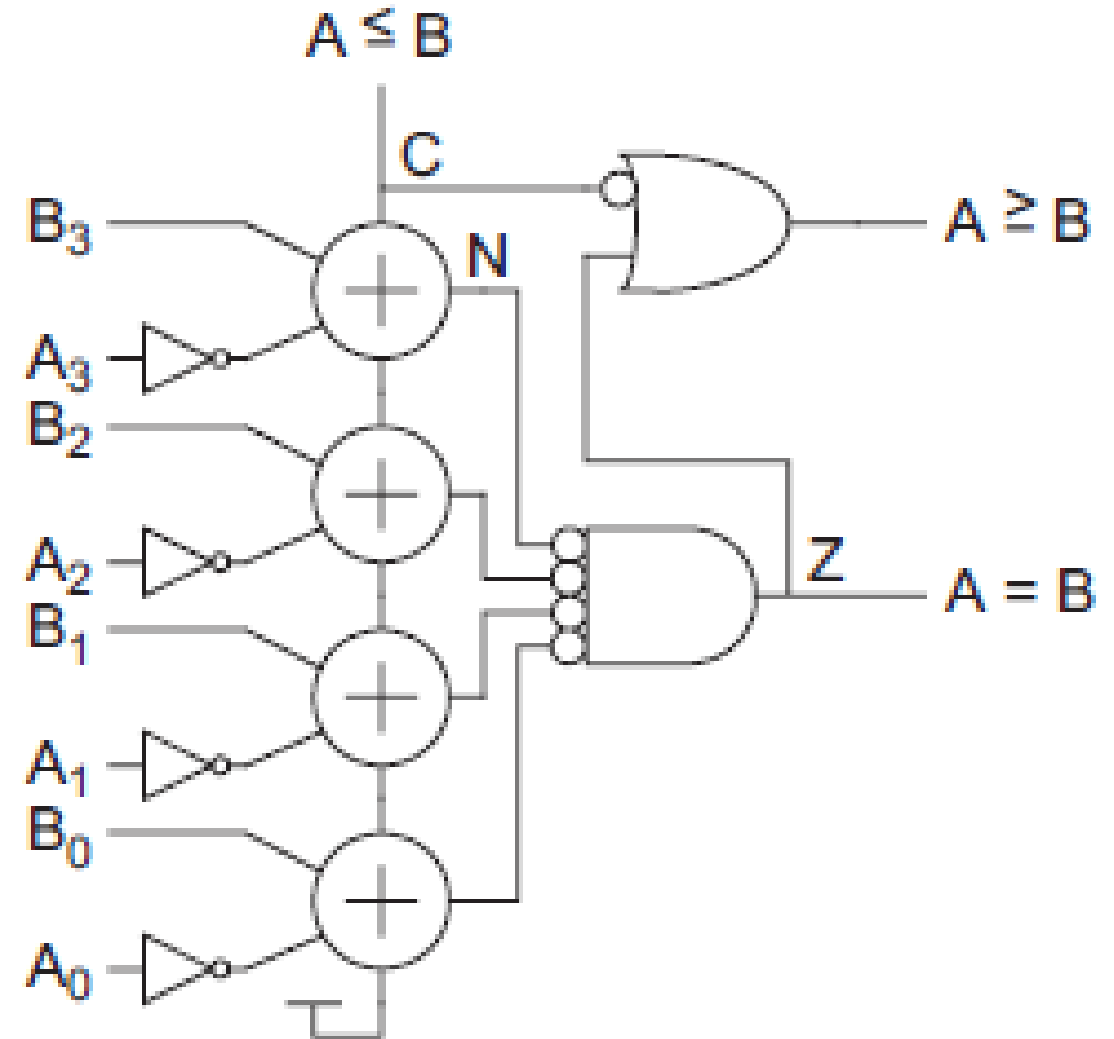
## 1) Magnitude Comparator

- A magnitude comparator determines the larger of two binary numbers.
- To compare two unsigned numbers A and B, **compute  $B - A = B + A + 1$** .
  - **If there is a carry-out,  $A \leq B$ ;**
  - **otherwise,  $A > B$ .**
  - **A zero detector indicates that the numbers are equal.**




Unsigned magnitude comparator

Table 8.4 Magnitude comparison		
Relation	Unsigned Comparison	Signed Comparison
$A = B$	$Z$	$Z$
$A \neq B$	$\overline{Z}$	$\overline{Z}$
$A < B$	$\overline{C + Z}$	$\overline{(N \oplus V) + Z}$
$A > B$	$\overline{C}$	$(N \oplus V)$
$A \leq B$	$C$	$\overline{(N \oplus V)}$
$A \geq B$	$\overline{C} + Z$	$(N \oplus V) + Z$

- Comparing signed two's complement numbers is complicated - possibility of overflow when subtracting two numbers with different signs.
- Must determine if the result is negative (N, indicated by the most significant bit of the result) and if it overflows the range of possible signed numbers. **overflow signal V.**
- If the inputs had different signs and the output sign is different from the sign of B. Then, **V** is true
- The actual sign of the difference  $B - A$  is  $S = N \oplus V$  because overflow flips the sign.
- If this corrected sign is negative ( $S = 1$ ), we know  $A > B$ .
 
## 2) Equality Comparator

- An equality comparator determines if  $(A = B)$ .
- This can be done more simply and rapidly with XNOR gates and a ones detector



### 3) $K = A + B$ Comparator

- Used in sum addressed memory
- This comparison can be done faster than computing  $A + B$  because **no carry propagation is necessary.**
- The **key** is that if you know  $A$  and  $B$ , you also know what the carry into each bit must be if  $K = A + B$ .
- you only need to check adjacent pairs of bits
  - **verify that the previous bit produces the carry required by the current bit**
  - **use a ones detector to check that the condition is true for all  $N$  pairs.**

$k = A + B$


$A_i$	$B_i$	$K_i$	$C_{i-1}$ (required)	$C_i$ (produced)
0	0	0	0 ✓	0
0	0	1	1 ✓	0
0	1	0	1 ✓	1 ✓
0	1	1	0 ✓	0
1	0	0	1 ✓	1 ✓
1	0	1	0	0
1	1	0	0	1 ✓
1	1	1	1	1 ✓

• Required carry,  $C_{i-1} = A_i \oplus B_i \oplus K_i$

• Produced carry,  $C_i = \bar{A} B \bar{K} + A \bar{B} \bar{K} +$
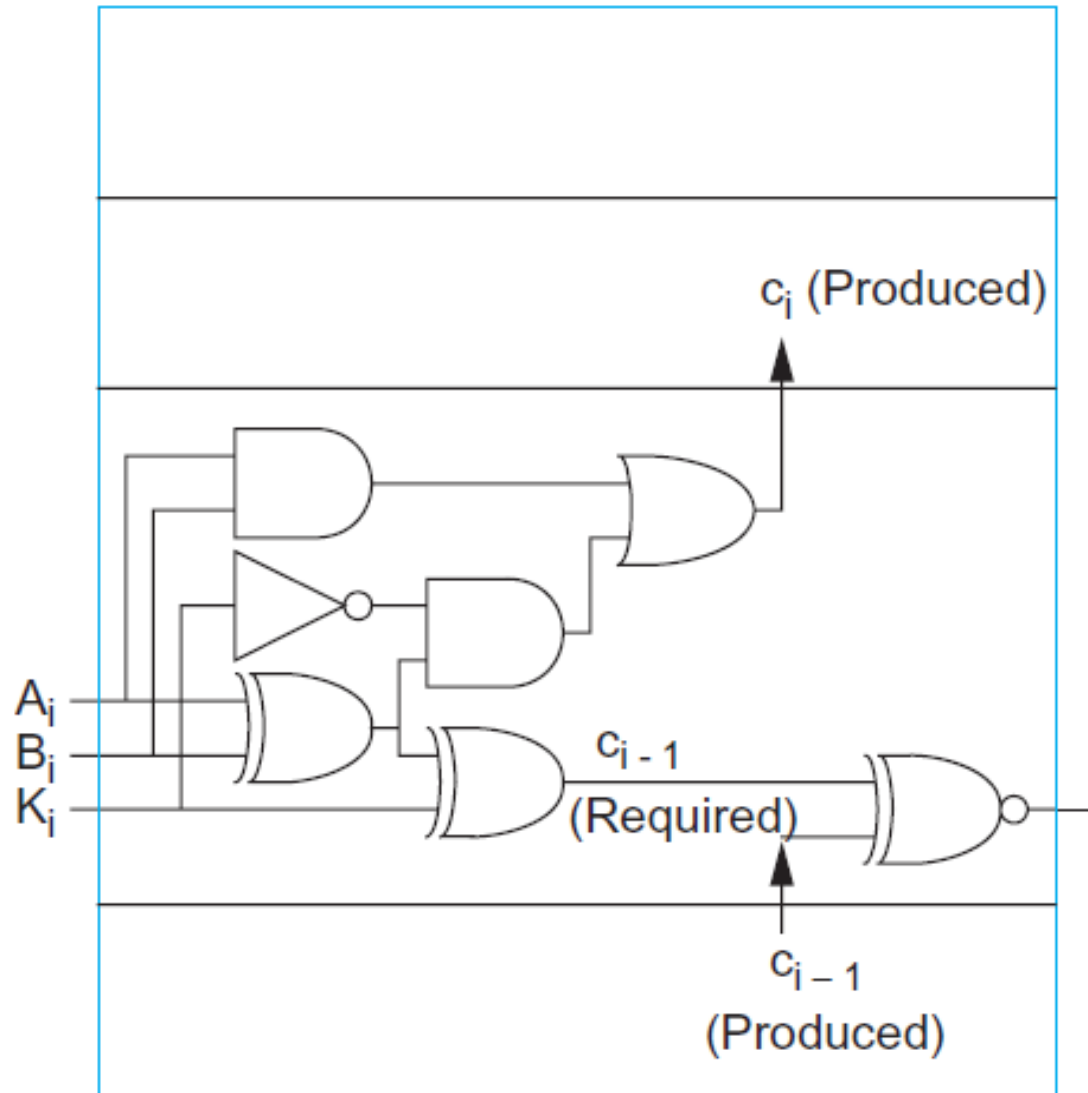
$$= \bar{K} (\bar{A} B + A \bar{B}) + AB(K + \bar{K}) = \bar{K} (A \oplus B) + AB$$






$A + B = K$  comparator

- **XNOR gate** is used to make sure that the **required carry matches the produced carry** at each bit position

# LFSR

- Linear Feedback Shift Registers
- consists of N registers configured as a shift register.
- input to the shift register comes from the XOR of particular bits of the register
- On reset, the registers must be initialized to a nonzero value (e.g., all 1s)

 


**FIGURE 11.54** 3-bit LFSR


**TABLE 11.7** LFSR sequence

Cycle	$Q_0$	$Q_1$	$Q_2 / Y$
0	1	1	1
1	0	1	1
2	0	0	1
3	1	0	0
4	0	1	0
5	1	0	1
6	1	1	0
7	1	1	1
Repeats forever			


- LFSR is an example of a ***maximal-length shift register*** because its output sequences through all  $2^n - 1$  combinations.
- The inputs fed to the XOR are called the **tap sequence** and are often specified with a **characteristic polynomial**.
- For example, this 3-bit LFSR has the characteristic polynomial  $1 + x^2 + x^3$  because the taps come after the second and third registers.
- characteristic polynomial **defined by XOR positions**

 

**FIGURE 11.54** 3-bit LFSR

 

$$P(x) = 1 + x + x^3 + x^4$$

 

$$P(x) = 1 + x^1 + x^6 + x^7 + x^8$$

- LFSRs are used for **high-speed counters** and **pseudo-random number generators**.
  - pseudo-random sequences are handy for built-in self-test and bit-error-rate testing in communications links
  - many spread spectrum communications systems such as GPS and CDMA


For certain lengths,  $N$ , more than two taps

**TABLE 11.8** Characteristic polynomials

$N$	Polynomial
3	$1 + x^2 + x^3$
4	$1 + x^3 + x^4$
5	$1 + x^3 + x^5$
6	$1 + x^5 + x^6$
7	$1 + x^6 + x^7$
8	$1 + x^1 + x^6 + x^7 + x^8$
9	$1 + x^5 + x^9$
15	$1 + x^{14} + x^{15}$
16	$1 + x^4 + x^{13} + x^{15} + x^{16}$
23	$1 + x^{18} + x^{23}$
24	$1 + x^{17} + x^{22} + x^{23} + x^{24}$
31	$1 + x^{28} + x^{31}$
32	$1 + x^{10} + x^{30} + x^{31} + x^{32}$
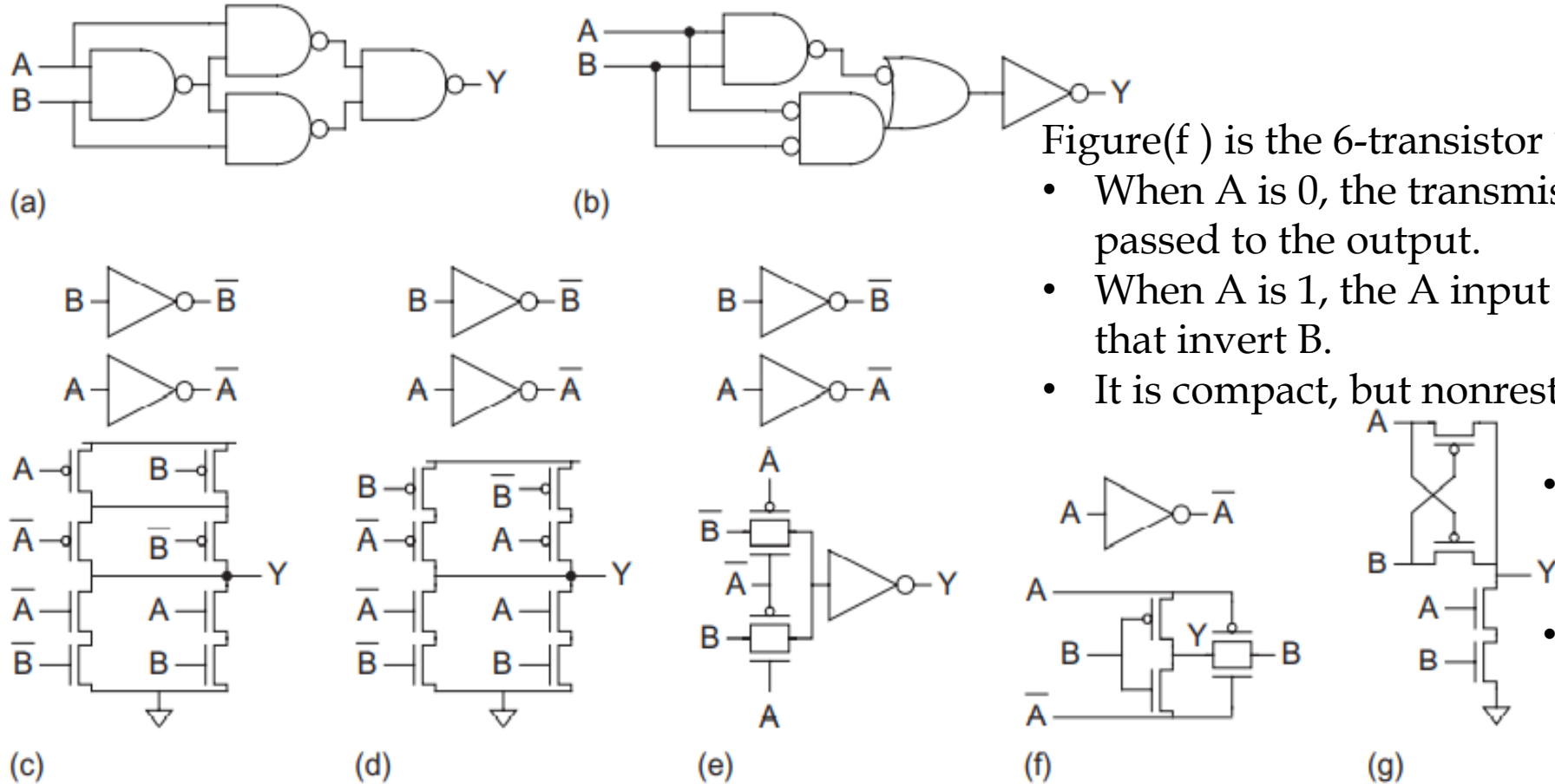
# XOR/XNOR circuit forms

- One of the chronic difficulties in CMOS circuit design is to construct a fast, compact, low-power XOR or XNOR gate



Figure(f) is the 6-transistor "invertible inverter" design.

- When A is 0, the transmission gate turns on and B is passed to the output.
- When A is 1, the A input powers a pair of transistors that invert B.
- It is compact, but nonrestoring.

- switch-level simulators cannot handle this unconventional design.
- Figure (g) [Wang94] is a compact and fast 4-transistor pass-gate design, but does not swing rail to rail.

**FIGURE 11.59** Static 2-input XOR designs



XOR gates with 3 or 4 inputs can be **more compact**, although **not necessarily faster** than a cascade of 2-input gates.

