

FUNDAMENTALS OF VLSI DESIGN

(19EC6DCFOV)

Module-2

Circuit Design Processes: MOS layers, Stick diagrams, Design rules and layout – lambda-based design and other rules. Examples. (Text book-1)

CMOS Sub System Design: Introduction, Addition/Subtraction, Single bit addition, Full adder design, Comparators, LFSR,XOR/XNOR circuits (Text book-3)

Text books:

1. Douglas A. Pucknell, Kamran E., “Basic VLSI Design”, 3rd Edition, *PHI Publication*, India.
3. Neil H.E. Weste, Harris, Banerjee, “CMOS VLSI design”, *Pearson*, Third Edition, 2007.














MOS LAYERS

- MOS design aim – **turning a specification into masks** for processing silicon to meet the specification.
- Four basic layers
 - n- diffusion
 - p- diffusion
 - Polysilicon
 - Metal
- **Isolated from one another** by thick or thin (thinox) silicon dioxide insulating layers.
- **Polysilicon and thinox regions interact** so that a **transistor is formed** where they cross one another.
- The **thin oxide (thinox) mask region** includes **n-diffusion, p-diffusion, and transistor channels.**
- **Contacts** are **used to join the layers**



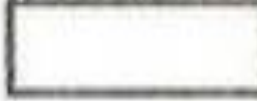








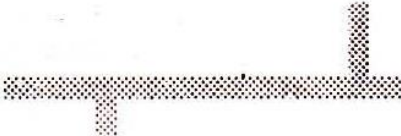

STICK DIAGRAMS

- Stick diagrams are used **to convey layer information through the use of a colour code.**
- Example, for CMOS design,
 - green for n-diffusion
 - Yellow/Brown for p-diffusion
 - red for polysilicon
 - blue for metal
 - black for contact areas
- **Color coding** has been **complemented by monochrome encoding** of the lines.


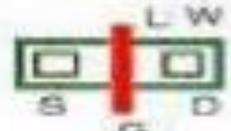
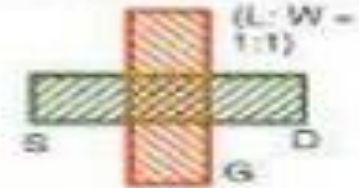



NMOS technology







COLOR	STICK ENCODING	LAYERS	MASK LAYOUT ENCODING
GREEN		n-diffusion (n ⁺ active) Thinox*	 *Thinox = n-diff. + transistor channels
RED		Polysilicon	
BLUE		Metal 1	
BLACK		Contact cut	
GRAY	NOT APPLICABLE	Overglass	
nMOS ONLY YELLOW		Implant	
pMOS ONLY BROWN		Buried contact	

Encodings for a simple metal nMOS process

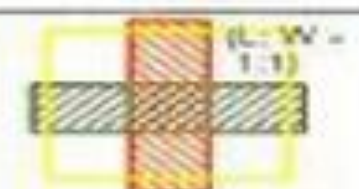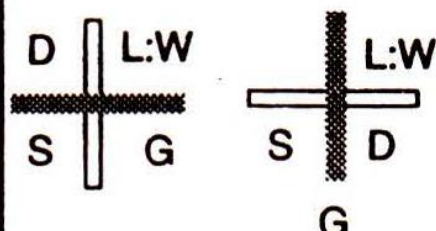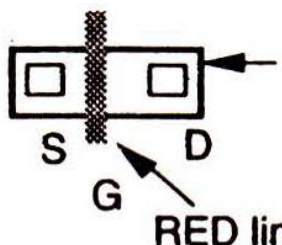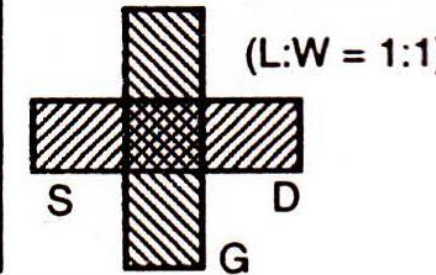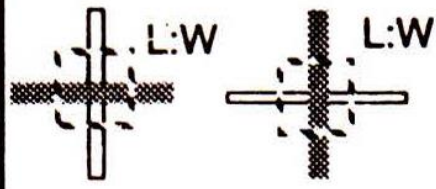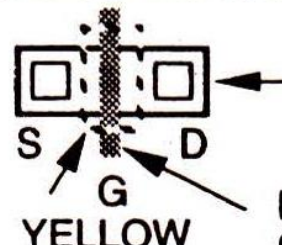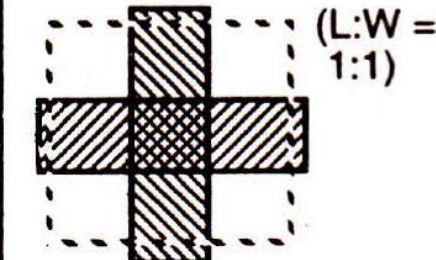
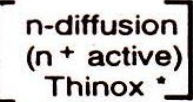





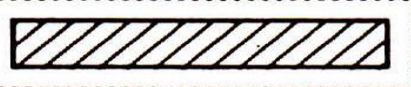

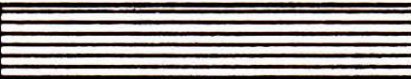



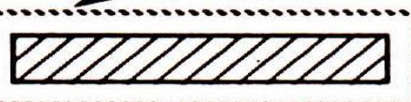

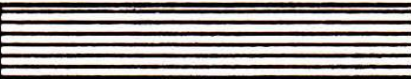



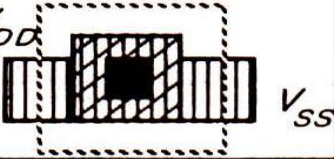
COLOR	STICK ENCODING	LAYERS	MASK LAYOUT ENCODING
	MONOCHROME		MONOCHROME
GREEN		n-diffusion (n ⁺ active) Thinox *	
RED		Polysilicon	
BLUE		Metal 1	
BLACK		Contact cut	
GRAY	NOT APPLICABLE	Overglass	
nMOS ONLY YELLOW		Implant	
nMOS ONLY BROWN		Buried contact	

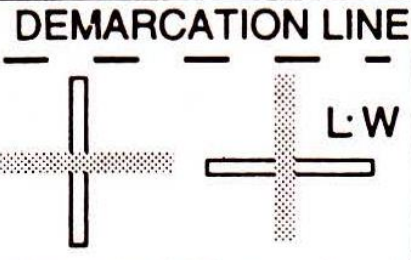
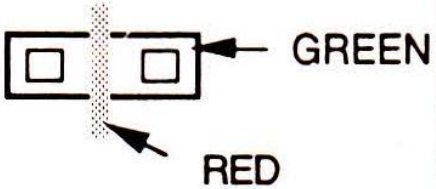
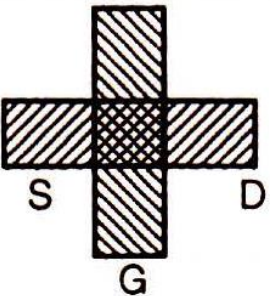

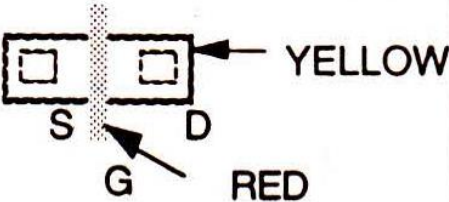
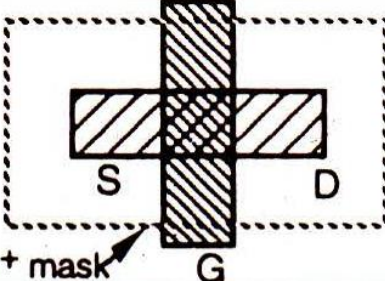
* Thinox = n-diff. + transistor channels

FEATURE	FEATURE (STICK)	FEATURE (SYMBOL)	FEATURE (MASK)
n-type enhancement mode transistor			
n-type depletion mode transistor nMOS only			
Source, drain and gate labeling will not normally be shown.			

FEATURE	FEATURE (STICK) (MONOCHROME)	FEATURE (SYMBOL) (MONOCHROME)	FEATURE (MASK) (MONOCHROME)
<i>n-type enhancement mode transistor</i>		 GREEN outline (COLOR) RED line (COLOR)	 (L:W = 1:1)
Transistor length to width ratio L:W should be shown but source, drain and gate labeling will not normally be shown.			
<i>n-type depletion mode transistor</i> nMOS ONLY		 GREEN outline (COLOR) RED line (COLOR) YELLOW (COLOR)	 (L:W = 1:1)

Encodings for CMOS process

COLOR	STICK ENCODING	LAYERS	MASK LAYOUT ENCODING
GREEN	MONOCHROME  ENCODING AS IN FIGURE 3-1(a)	 n-diffusion (n ⁺ active) Thinox *	MONOCHROME * Thinox = n-diff. + p-diff. + transistor channels  ENCODING AS IN FIGURE 3-1(a)
RED		Polysilicon	
BLUE		Metal 1	
BLACK		Contact cut	
GRAY		Overglass	
GREEN IN P ⁺ (MASK)	 NOT SHOWN IN STICK DIAGRAM    DEMARICATION LINE p-well edge is shown as a demarcation line in stick diagrams  	p-diffusion (p ⁺ active)	      
YELLOW (STICK)		p ⁺ mask	
YELLOW			
DARK BLUE OR PURPLE		Metal 2	
BLACK		VIA	
BROWN		p-well	
BLACK		V _{DD} or V _{SS} CONTACT	

FEATURE	FEATURE (STICK) (MONOCHROME)	FEATURE (SYMBOL) (MONOCHROME)	FEATURE (MASK) (MONOCHROME)
<i>n-type enhancement mode transistor</i> (as in Figure 3-1(a)) Transistor length to width ratio L:W may be shown.			
<i>p-type enhancement mode transistor</i> Note: p-type transistors are placed above and n-type transistors below the demarcation line			







Steps for CMOS Process

- Draw the metal (Blue) Vdd and Vss rails in parallel and create a demarcation line between them. Allowing enough space between them for other circuit elements.
- N-Devices are placed below the demarcation line and P-device are placed above the demarcation line.
- N & P devices are then connected using metal, Polysilicon and contacts.
- Finally the remaining interconnections are made & control signals and data inputs are added.

Introduction

- Stick diagrams convey layer information in a chip.
- Interface between the circuit and the layout.
- Size of transistors, width of layers, wire length etc... are not mentioned in a stick diagram.
- For a chip designer, all CMOS designs consist of the following layers:
 - Substrate or wells of p-type for nMOS transistors and n-type for pMOS transistors
 - Diffusion layers, generally called as Active areas
 - Polysilicon layers, forms the Gate terminals
 - Metal and interconnect layers
 - Contact and via layers


Colour Codes & Patterns

Layers	Colour	Patterns
N diffusion	Green	
P diffusion	Yellow/Brown	
Polysilicon	Red	
Metal 1	Blue	
Metal 2	Magenta	
Contact & Taps	Black	


V_{DD} and V_{SS} - metal layers - Blue

Transistors using Colour Code



NMOS Transistor

 

PMOS Transistor

 

Example - CMOS Inverter

  

Important Note

- Diffusion paths must not cross the demarcation line.
- N & P diffusion wires must not join.
- The metal should be used to connect n & p features.
- We must place crosses (X) on Vdd and Vss rails to represent substrate and P-well connections respectively.
- Only metal & polysilicon can cross the demarcation line.
- Represent the Vss and Vdd contact crosses
 - One on Vdd line for every 4 P-transistors.
 - One on Vss line for every 4 N-transistors.
- Metal lines on different layers (M1 and M2) can cross one another. Contacting 2 metal lines requires a Via.

Steps for NMOS Process

- Draw the metal Vdd and Vss rails in parallel and create a demarcation line between them. Allowing enough space between them for other circuit elements.
- Draw the diffusion paths between the rails.
- Pull up device (depletion type) is to be connected from the output point (Source) to Vdd (Drain)
- Pull down device (enhancement type) is to be connected from the output point (Drain) to Ground (Source)

DESIGN RULES AND LAYOUT

- The **object** of a set of design rules is **to allow** a ready **translation of circuit design concepts**, usually **in stick diagram** or symbolic form, **into actual geometry in silicon**.
- The design rules are the **effective interface between the circuit/system designer and the fabrication engineer**.
- 2-ways
 - μ metal based design rules (orbit)
 - Lambda-based Design Rules
 - **straightforward**
 - **relatively simple to apply**

- Design rules are the communication link between the designer specific requirements and the fabricator (metalizing the design)
- Design rules are workable mask layers from which the various layer in silicon.

Layout Design Rules


- ◆ **Width** - the minimum width of a rectangle
- ◆ **Spacing** - the minimum spacing between two rectangles on the same or different layers
- ◆ **Overlap** - specifies how much a rectangle must surround another on another layer

$$\lambda = \frac{\text{channel length (L)}}{2}$$

Design Rules




METAL

 

DIFFUSION




POLYSILICON

 

Design Rules




METAL

 

DIFFUSION




POLYSILICON

 

Design Rules




METAL

 

DIFFUSION



POLYSILICON

 

Design Rules





METAL




POLYSILICON




Design Rules

  


Different layers for Layout

 


Poly Silicon

 


n-diff

 

P-diff

 

M1

 

M2

Lambda-based Design Rules


 



Figure 3–6 Design rules for wires (nMOS and CMOS)

Minimum size transistors



 


1. Metal 1 to polysilicon or to diffusion

3λ minimum

 

   
$2\lambda \times 2\lambda$ cut centered
on $4\lambda \times 4\lambda$ superimposed
areas of layers to be joined
in all cases



2λ 2λ
Minimum separation
Multiple cuts

2. Via (contact from metal 2 to metal 1 and thence to other layers)

Metal 2

 


Metal 1

2λ minimum separation
(if other spacings allow)

$4\lambda \times 4\lambda$ area of overlap with
 $2\lambda \times 2\lambda$ via at center

 Via and cut used to
connect metal 2 to
diffusion



CMOS Sub System Design

Introduction

Partitioning the system into subsystems of the types listed below:


- Datapath operators
- Memory elements
- Control structures
- Special-purpose cells
 - I/O
 - Power distribution
 - Clock generation and distribution
 - Analog and RF

Addition/Subtraction

- Basis for many processing operations- counting, multiplication, filtering etc..
- add two binary numbers
- adder architectures serve different speed/power/area requirements


Single bit addition

1) Half adder

 


<i>A</i>	<i>B</i>	<i>C_{out}</i>	<i>S</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0
 
$$S = A \oplus B$$
$$C_{\text{out}} = A \cdot B$$



2) Full adder

 

A	B	C	G	P	K	C _{out}	S
0	0	0	0	0	1	0	0
		1				0	1
0	1	0	0	1	0	0	1
		1				1	0
1	0	0	0	1	0	0	1
		1				1	0
1	1	0	1	0	0	1	0
		1				1	1

Generate (G): The adder generates a carry when Cout is true independent of Cin

$$G = A \cdot B.$$

Propagate (P): The adder propagates a carry; i.e., it produces a carry-out if and only if it receives a carry-in

$$P = A \oplus B.$$

Kill (K): The adder kills a carry when Cout is false independent of Cin

$$K = \bar{A} \cdot \bar{B} = \overline{A + B}$$

A	B	C_i	S	C_o	<i>Carry status</i>
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

For S:

Full adder design

		BC_{in}			
A		$\overline{B}\overline{C}_{in}$	$\overline{B}C_{in}$	BC_{in}	$B\overline{C}_{in}$
	\overline{A}		1		1
A		1		1	

$$S = A \oplus B \oplus C_{in}$$

$$S = \overline{A}\overline{B}C_{in} + \overline{A}B\overline{C}_{in} + \underline{\underline{AB\overline{C}_{in}}} + \underline{\underline{\overline{A}BC_{in}}}$$

$$S = \overline{\overline{A}\overline{B}\overline{C}_{in}} \cdot \overline{\overline{A}\overline{B}C_{in}} \cdot \overline{AB\overline{C}_{in}} \cdot \overline{\overline{A}BC_{in}}$$

$$= \underbrace{(\overline{A+B+C_{in}})} \cdot \underbrace{(A+B+\overline{C_{in}})} \cdot \underbrace{(\overline{A+B+C_{in}})} \cdot \underbrace{(A+B+C_{in})}$$

		BC_{in}			
A	\overline{A}	$\overline{B}\overline{C}_{in}$	$\overline{B}C_{in}$	BC_{in}	$B\overline{C}_{in}$
	A		1	1	1

$$C_{out} = \overline{A}B + BC_{in} + C_{in}A$$

$$\begin{aligned}
 C_{out} &= \overline{A}B + \overline{B}C_{in} + \overline{C_{in}A} \\
 &= (\overline{A} + \overline{B}) \cdot (\overline{B} + \overline{C_{in}}) \cdot (\overline{C_{in}} + \overline{A})
 \end{aligned}$$

Common procedure used for all type of circuits:

NMOS


OR operation (+)
AND operation (.)

parallel
series

PMOS

OR operation (+)
AND operation (.)

series
parallel




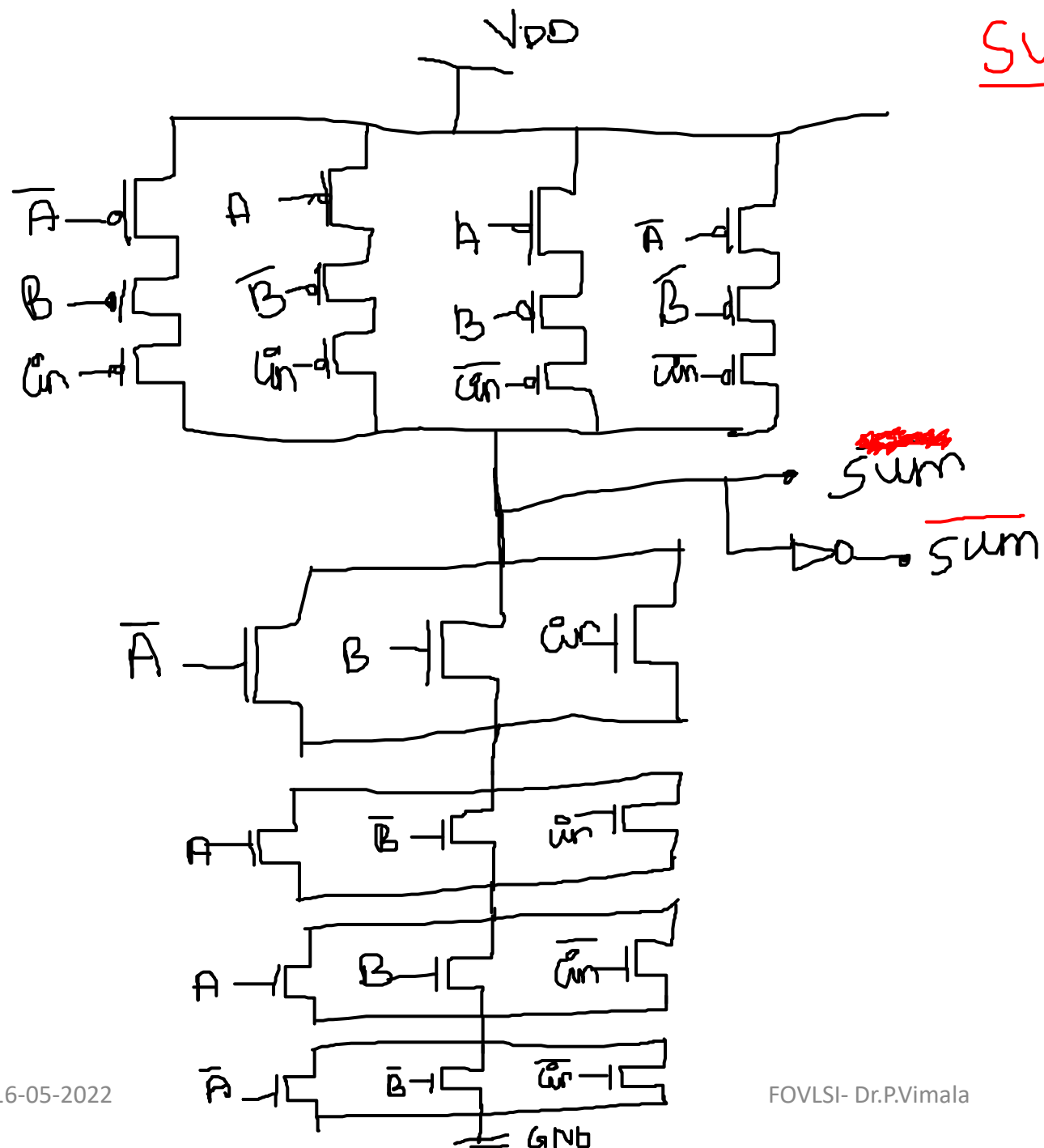


sum

No of transistors

24 ~~24~~

24

    

32 transistors (6 for the inverters, 10 for the majority gate, and 16 for the 3-input XOR).

A	B	C	G	P	K	C _{out}	S
0	0	0	0	0	1	0	0
		1				0	1
0	1	0	0	1	0	0	1
		1				1	0
1	0	0	0	1	0	0	1
		1				1	0
1	1	0	1	0	0	1	0
		1				1	1

BC_{in}

A

	$\overline{B}\overline{C}_{in}$	$\overline{B}C_{in}$	BC_{in}	$B\overline{C}_{in}$
\overline{A}			1	
A		1	1	1

$$C_{out} = AB + BC_{in} + C_{in}A$$

$$C_{out} = AB + C_{in}(A + B) \checkmark$$

$$S = C_{in}\overline{C_{out}} + B\overline{C_{out}} + A\overline{C_{out}} + ABC_{in}$$


$$S = \overline{C_{out}}[A + B + C_{in}] + ABC_{in}$$


A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1 ✓
0	1	0	0	1 ✓
0	1	1	1	0
1	0	0	0	1 ✓
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1 ✓


$$C_{out} = AB + C_{in}(A+B)$$

$$S = AB\bar{C}_{in} + \bar{C}_{out}(A+B+C_{in})$$

28

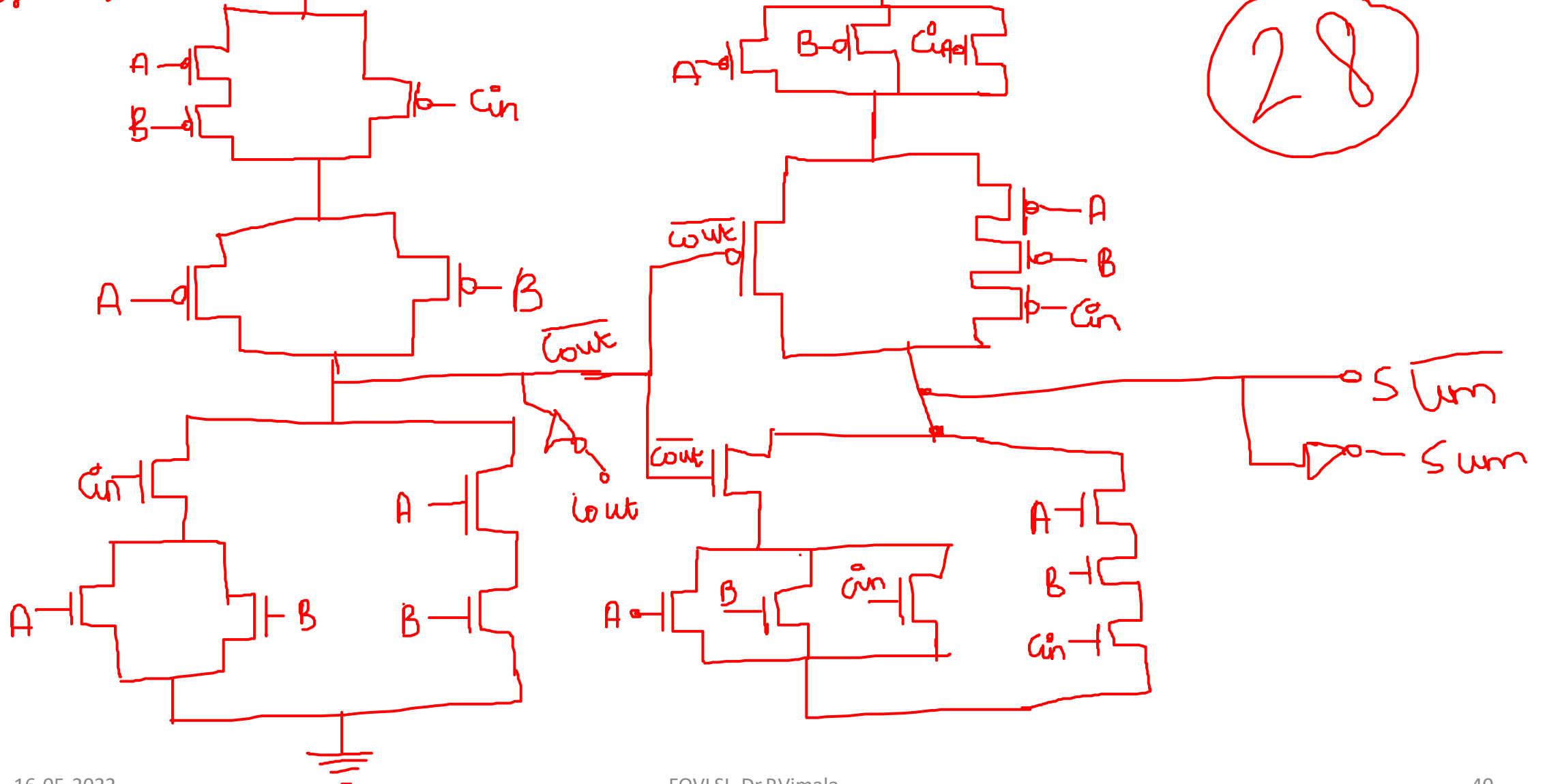

 

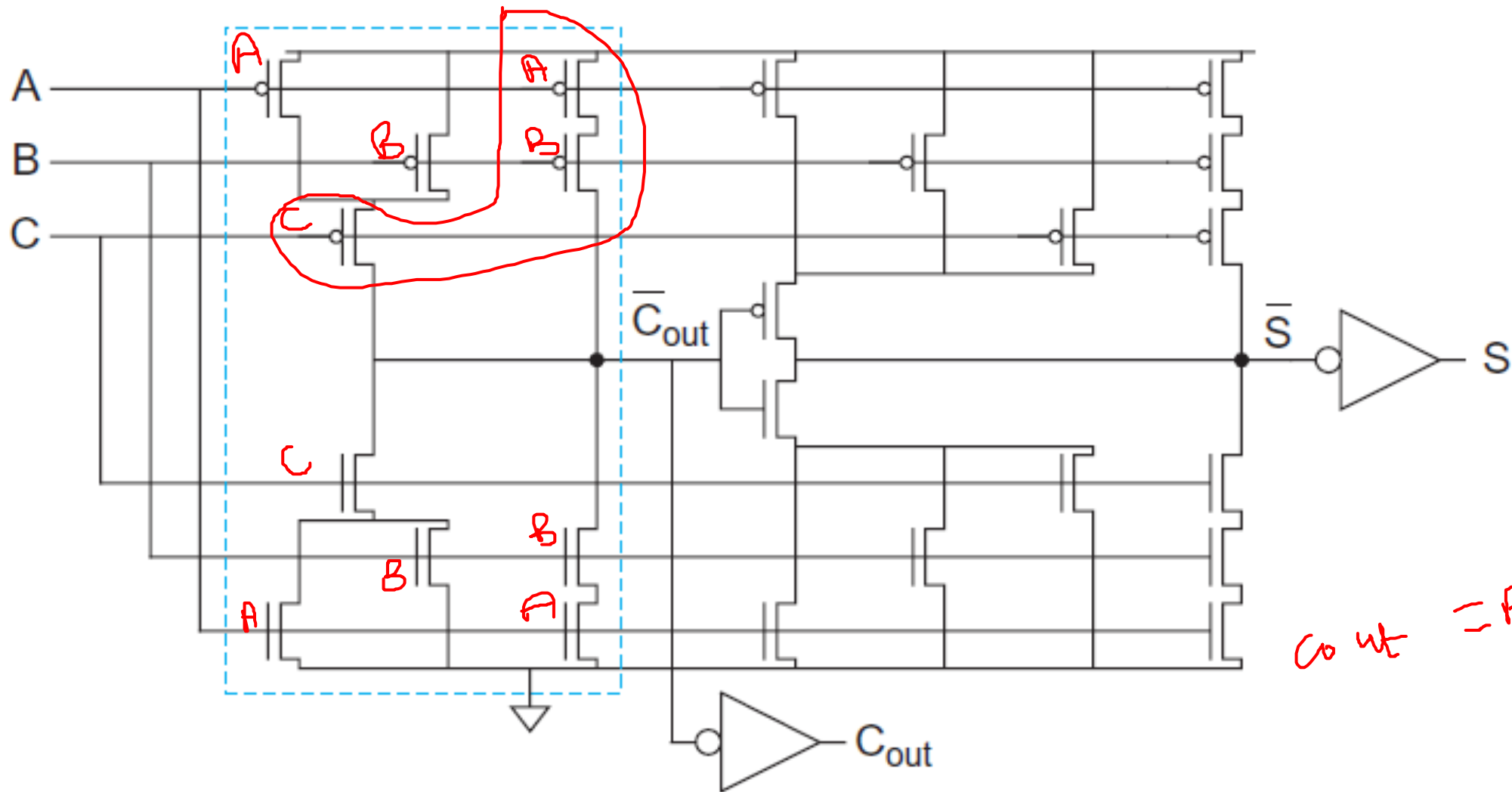


pMOS network is identical to the nMOS network rather than being the conduction complement, so the topology is called a **mirror adder**.

Comparators

 1) Magnitude Comparator

- A magnitude comparator determines the larger of two binary numbers.
- To compare two unsigned numbers A and B, **compute $B - A = B + A + 1$** .
 - **If there is a carry-out, $A \leq B$;**
 - **otherwise, $A > B$.**
 - **A zero detector indicates that the numbers are equal.**




Unsigned magnitude comparator

Table 8.4 Magnitude comparison		
Relation	Unsigned Comparison	Signed Comparison
$A = B$	Z	Z
$A \neq B$	\overline{Z}	\overline{Z}
$A < B$	$\overline{C + Z}$	$\overline{(N \oplus V) + Z}$
$A > B$	\overline{C}	$(N \oplus V)$
$A \leq B$	C	$\overline{(N \oplus V)}$
$A \geq B$	$\overline{C} + Z$	$(N \oplus V) + Z$

- Comparing signed two's complement numbers is complicated - possibility of overflow when subtracting two numbers with different signs.
- Must determine if the result is negative (N, indicated by the most significant bit of the result) and if it overflows the range of possible signed numbers. **overflow signal V.**
- If the inputs had different signs and the output sign is different from the sign of B. Then, **V** is true
- The actual sign of the difference $B - A$ is $S = N \oplus V$ because overflow flips the sign.
- If this corrected sign is negative ($S = 1$), we know $A > B$.

 2) Equality Comparator

- An equality comparator determines if $(A = B)$.
- This can be done more simply and rapidly with XNOR gates and a ones detector



3) $K = A + B$ Comparator

- Used in sum addressed memory
- This comparison can be done faster than computing $A + B$ because **no carry propagation is necessary.**
- The **key** is that if you know A and B , you also know what the carry into each bit must be if $K = A + B$.
- you only need to check adjacent pairs of bits
 - **verify that the previous bit produces the carry required by the current bit**
 - **use a ones detector to check that the condition is true for all N pairs.**


$k = A + B$

A_i	B_i	K_i	C_{i-1} (required)	C_i (produced)
0	0	0	0 ✓	0
0	0	1	1 ✓	0
0	1	0	1 ✓	1 ✓
0	1	1	0 ✓	0
1	0	0	1 ✓	1 ✓
1	0	1	0	0
1	1	0	0	1 ✓
1	1	1	1	1 ✓

• Required carry, $C_{i-1} = A_i \oplus B_i \oplus K_i$

• Produced carry, $C_i = \bar{A} B \bar{K} + A \bar{B} \bar{K} +$
 
$$= \bar{K} (\bar{A} B + A \bar{B}) + A B (K + \bar{K}) = \bar{K} (A \oplus B) + A B$$



$A + B = K$ comparator

- **XNOR gate** is used to make sure that the **required carry matches the produced carry** at each bit position

LFSR

- Linear Feedback Shift Registers
- consists of N registers configured as a shift register.
- input to the shift register comes from the XOR of particular bits of the register
- On reset, the registers must be initialized to a nonzero value (e.g., all 1s)

 


FIGURE 11.54 3-bit LFSR

TABLE 11.7 LFSR sequence

Cycle	Q_0	Q_1	Q_2 / Y
0	1	1	1
1	0	1	1
2	0	0	1
3	1	0	0
4	0	1	0
5	1	0	1
6	1	1	0
7	1	1	1
Repeats forever			

- LFSR is an example of a ***maximal-length shift register*** because its output sequences through all $2^n - 1$ combinations.
- The inputs fed to the XOR are called the **tap sequence** and are often specified with a **characteristic polynomial**.
- For example, this 3-bit LFSR has the characteristic polynomial $1 + x^2 + x^3$ because the taps come after the second and third registers.
- characteristic polynomial **defined by XOR positions**



 


FIGURE 11.54 3-bit LFSR

 

$$P(x) = 1 + x + x^3 + x^4$$

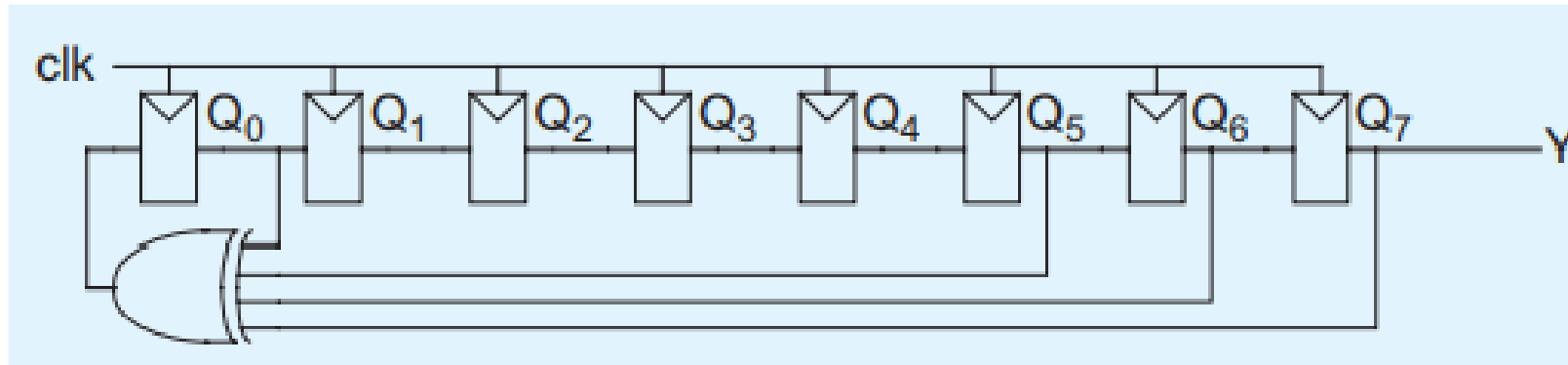

$$P(x) = 1 + x^1 + x^6 + x^7 + x^8$$

- LFSRs are used for **high-speed counters** and **pseudo-random number generators**.
 - pseudo-random sequences are handy for built-in self-test and bit-error-rate testing in communications links
 - many spread spectrum communications systems such as GPS and CDMA


For certain lengths, N , more than two taps

TABLE 11.8 Characteristic polynomials


N	Polynomial
3	$1 + x^2 + x^3$
4	$1 + x^3 + x^4$
5	$1 + x^3 + x^5$
6	$1 + x^5 + x^6$
7	$1 + x^6 + x^7$
8	$1 + x^1 + x^6 + x^7 + x^8$
9	$1 + x^5 + x^9$
15	$1 + x^{14} + x^{15}$
16	$1 + x^4 + x^{13} + x^{15} + x^{16}$
23	$1 + x^{18} + x^{23}$
24	$1 + x^{17} + x^{22} + x^{23} + x^{24}$
31	$1 + x^{28} + x^{31}$
32	$1 + x^{10} + x^{30} + x^{31} + x^{32}$

XOR/XNOR circuit forms

 
- One of the chronic difficulties in CMOS circuit design is to construct a fast, compact, low-power XOR or XNOR gate




(a)

 


(b)

 


(c)

 

(d)

 


(e)

 


Figure(f) is the 6-transistor “invertible inverter” design.

 - When A is 0, the transmission gate turns on and B is passed to the output.
- When A is 1, the A input powers a pair of transistors that invert B.
- It is compact, but nonrestoring.



(f)

 


(g)

- switch-level simulators cannot handle this unconventional design.
- Figure (g) [Wang94] is a compact and fast 4-transistor pass-gate design, but does not swing rail to rail.

FIGURE 11.59 Static 2-input XOR designs

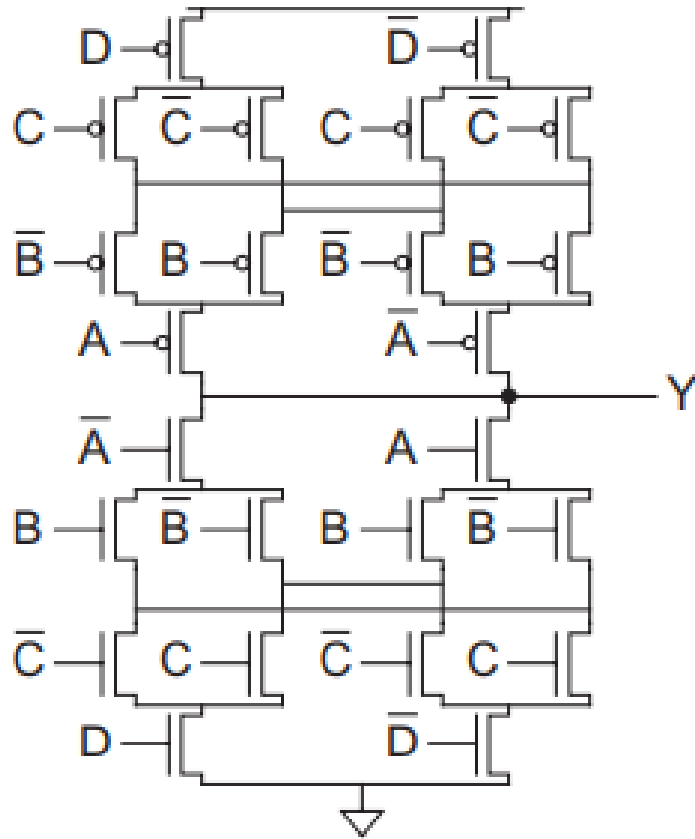XOR gates with 3 or 4 inputs can be **more compact**, although **not necessarily faster** than a cascade of 2-input gates.



4 input CMOS XOR